

Concept Question 1-4: What is the difference between the symbol for a dc voltage source and that for an ac source?

A dc source is represented by either  or , whereas an ac source is represented by .