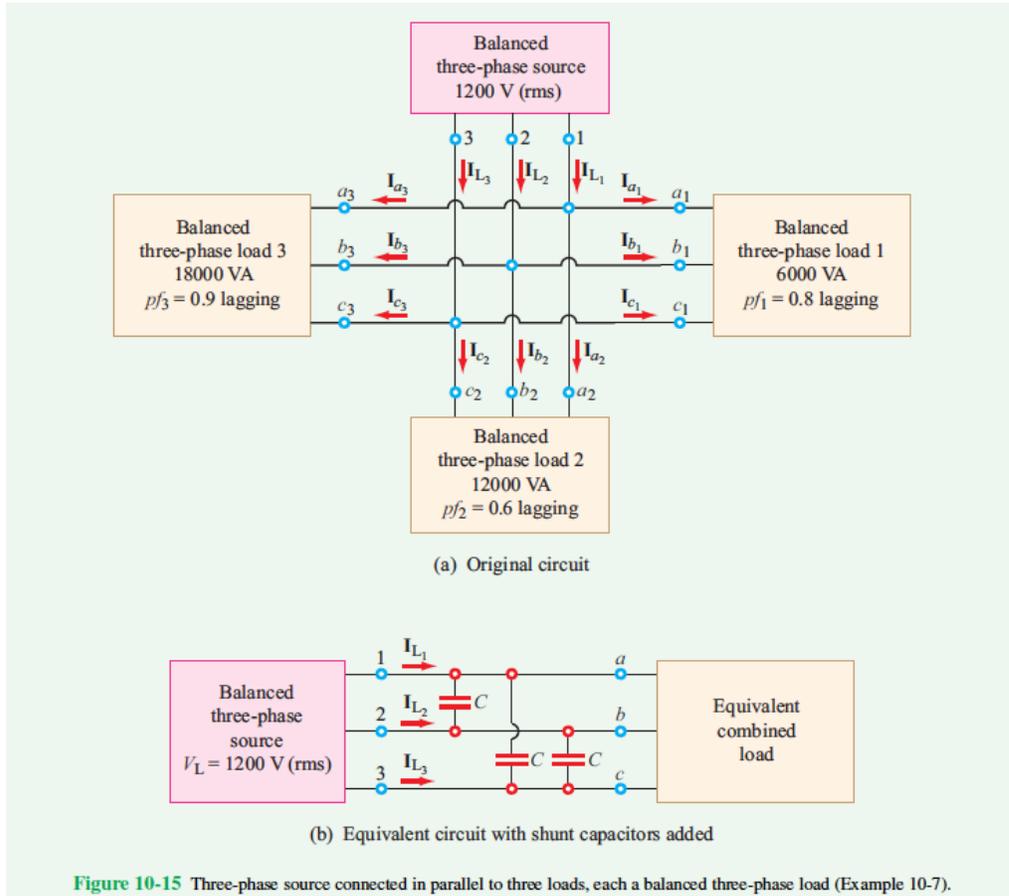


**Concept Question 10-11:** How can one apply the  $pf$ -compensation method to a three-phase source connected in parallel to multiple, balanced, three-phase load circuits?

See the illustration in Fig. 10-15.



**Figure 10-15** Three-phase source connected in parallel to three loads, each a balanced three-phase load (Example 10-7).