

**Concept Question 11-4:** How is the mutual inductance  $M$  related to  $L_1$  and  $L_2$  for a perfectly coupled transformer?

$$M(\text{max}) = \sqrt{L_1 L_2}. \quad (11.22)$$

(perfectly coupled transformer with  $k = 1$ )