

Concept Question 11-6: What is the coupling coefficient of an ideal transformer?

$k = 1$ for an ideal transformer.