

Concept Question 2-1: If the terminals of the battery in Fig. 2-6 were corroded, how would that change the problem and the results?

If the terminals of the battery are corroded, their resistance becomes significant relative to the cables, in which case less power makes it to the motor.