

Concept Question 2-10: When is the Y-transformation used? Describe the inherent symmetry between the resistance values of the Y circuit and those of the delta circuit.

The Y-transformation is used when a node is connected to three branches each containing a resistor.

