

Concept Question 2-7: What conditions must be satisfied in order for two circuits to be considered equivalent?

▶ Two circuits connected between a pair of nodes are considered to be equivalent—as seen by the rest of the circuit—if they exhibit identical $i-v$ characteristics at those nodes. ◀