

Concept Question 3-1: The node-voltage method relies on the application of Kirchhoff's current law. Explain.

The node-voltage method adds all the currents entering a node in terms of the voltage between that node and the voltages of the nodes between which the resistors reside.

