

Concept Question 3-14: Under what conditions is the power transferred from a power source to a load resistor a maximum? When is the voltage a maximum? When is the current a maximum?

Power transfer is maximum when load resistance equals source resistance. Voltage transfer is maximum when load resistance is infinite (open circuit).

Current transfer is maximum when load resistance is zero (short circuit).