

Concept Question 3-15: Of the power generated by an input circuit, what is the maximum fraction that can be transferred to an external load?

50%