

Concept Question 3-16: How is the collector current related to the base current in a BJT?

$$I_C = \beta I_B, \quad (3.45)$$

where β is a transistor parameter called the *common-emitter current gain*.