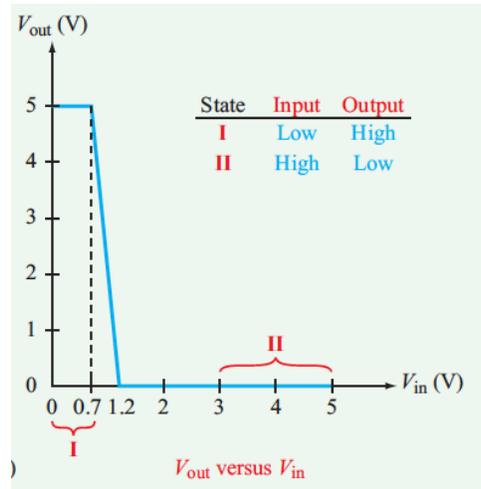


Concept Question 3-17: What is a digital inverter? How are its input and output voltages related to one another?



A digital inverter converts a high voltage (representing digital 1) into a low voltage (representing digital 0), and vice versa.