

**Concept Question 3-2:** Why does a circuit with  $n_{\text{ex}}$  extraordinary nodes require only  $(n_{\text{ex}} - 1)$  node-voltage equations to analyze it?

Because one of the nodes is used as the reference (ground) node with zero voltage.