

Concept Question 3-3: What impact does the presence of a dependent source have on the implementation of the node-voltage method?

The solution method remains applicable, but an auxiliary relation is needed describing the dependent current or voltage source.