

**Concept Question 3-5:** How does the presence of a dependent source in the circuit influence the implementation procedure of the mesh-current method?

The presence of a dependent source in a circuit does not alter the basic procedure of the mesh-current method, but it requires the addition of a supplemental equation expressing the relationship between the dependent source and the other parts of the circuit.