

Concept Question 3-8: If the circuit contains a mixture of real voltage and current sources, what step should be taken to prepare the circuit for application of one of the two by-inspection methods?

Either convert all current sources into voltage sources, or vice versa, so as to make all sources voltage sources or all sources current sources, prior to applying the relevant by-inspection method.