

Concept Question 4-13: What is an inverting adder?

An inverting adder is an inverting amplifier whose input and feedback resistances are chosen so that

$$v_o = -(v_1 + v_2)$$