

Concept Question 4-14: What is the function of a voltage follower, and why is it called a “buffer”?

A voltage follower is an op-amp circuit whose output voltage is equal to its input voltage. It is called a “buffer” because the output voltage is independent of both the input resistance and the load resistance, thereby making it immune to changes in the load resistance.