

Concept Question 4-15: How much voltage gain is provided by the voltage follower?

Voltage gain = 1.