

**Concept Question 4-16:** When designing a multistage op-amp circuit, what should the design engineer do to insure that none of the op amps is driven into saturation?

When designing and building a multistage circuit, designers usually insert buffers between adjacent stages, which allows them to design each stage separately and then cascade them all together with buffers in between them.