

Concept Question 4-18: In a digital-to-analog converter, what dictates the maximum value that R_f can assume?

The number of bits and the value of the saturation voltage.