

Concept Question 4-2: What is the difference between the op-amp gain A and the circuit gain G ?

Op-amp gain A refers to the inherent gain of the op-amp when not connected to circuit elements, whereas the circuit gain G is the gain for the entire circuit, including the op-amp and all elements connected to it.