

Concept Question 4-4: An op amp is characterized by three important input-output attributes. What are they?

The three important attributes are:

- The op-amp's open-loop gain A ,
- input resistance R_i , and
- output resistance R_o .