

Concept Question 4-5: Why is negative feedback used in op-amp circuits?

Positive feedback causes the op amp to saturate, thereby forcing its output voltage v_o to become equal to its supply voltage V_{cc} . Application of negative feedback reduces the output voltage to a level lower than V_{cc} , thereby offering a trade-off between circuit gain and dynamic range for the input voltage.