

Concept Question 4-8: What are the values of the input and output resistances of the ideal op amp?

$$R_i = \infty, \quad R_o = 0$$