

Concept Question 4-9: In the ideal op-amp model, R_o is set equal to zero. To satisfy such an approximation, does the load resistance need to be much larger or much smaller than R_o ? Explain.

The load resistance should be much larger than R_o , so that the role of R_o can be ignored by setting it equal to zero.