

Concept Question 5-17: What specific characteristic defines a first-order circuit?

Mathematically, the circuit is described by a first-order differential equation, and physically the circuit contains a single nonlinear element (capacitor or inductor), or multiple capacitors that can be reduced to a single capacitor, or multiple inductors that can be reduced to a single inductor.