

Concept Question 5-18: What does the time constant of an RC circuit represent? Would a larger capacitor discharge faster or more slowly than a small one?

The time constant defines how fast or slow the circuit responds to change. A larger capacitor means a longer time constant, and hence a slower response.