

Concept Question 5-19: For the natural response of an RC circuit, how does the decay rate for voltage compare with that for power?

Power decays twice as fast as voltage.