

Concept Question 5-20: What are the three quantities needed to establish $v_C(t)$ across a capacitor in an RC circuit?

The initial voltage $v_C(0)$, the final voltage $v_C(\infty)$, and the time constant $\tau = RC$.