

Concept Question 5-24: What causes clipping of the waveform at the output of an op-amp integrator circuit? Can clipping occur at the output of a differentiator circuit?

Clipping occurs whenever the output starts to exceed the supply voltage V_{cc} , which can occur in both the integrator circuit and the differentiator circuit.