

Concept Question 5-8: Explain why a capacitor behaves like an open circuit under dc conditions.

Since

$$i = C \frac{dv}{dt},$$

under dc conditions $dv/dt = 0$. Hence $i = 0$, which is equivalent to an open circuit that allows no current to flow through it.