

**Concept Question 6-1:** Determination of initial circuit conditions after a sudden change relies on two fundamental properties of capacitors and inductors. What are they?

The voltage  $v_C$  across a capacitor cannot change instantaneously, and neither can the current  $i_L$  through an inductor.