

**Concept Question 6-3:** What role do initial and final values play in the solution of a circuit?

Initial and final values determine the values of the constants in the solutions of the differential equations.