

Concept Question 6-6: A circuit contains two capacitors and three inductors, in addition to resistors and sources. Under what circumstance is it a second-order circuit?

It is a second-order circuit if the two capacitors can be combined into a single capacitor and the three inductors can be combined into a single inductor.