

Concept Question 7-12: If Z_{Th} of a certain circuit is purely imaginary, what would be your expectation about whether or not the circuit contains resistors?

If Z_{Th} of a circuit is purely imaginary, then the original circuit contains no resistors.