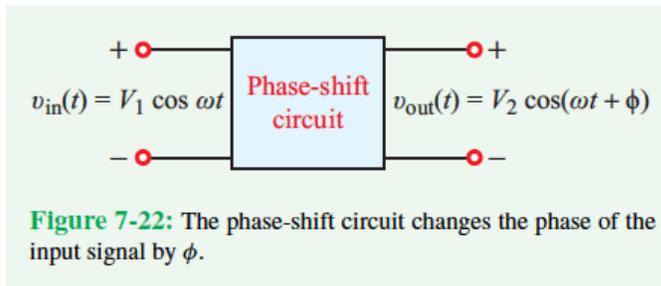


Concept Question 7-15: Describe the function of a phase-shift circuit in terms of time delay or time advance of the waveform.



The phase shift circuit shifts the phase by ϕ , corresponding to a time shift of

$$\Delta t = \left(\frac{\phi}{2\pi} \right) T$$

where T is the period.