

Concept Question 7-16: When is it necessary to use multiple stages to achieve the desired phase shift?

A single RC phase-shift circuit cannot shift the phase by more than 90° . The use of multiple stages allows us to shift the phase by more than 90° .