

Concept Question 7-18: For an ideal transformer, how is power p_2 related to power p_1 ?

They are equal.