

Concept Question 7-8: What type of circuit is equivalent to the behavior of (a) an inductor at dc and (b) a capacitor at very high frequencies?

- (a) An inductor at dc acts like a short circuit.
- (b) A capacitor at very high frequencies acts like a short circuit.