

**Concept Question 9-1:** Is the transfer function of a circuit always the same as its voltage gain?

No, it can be the ratio of any combination of voltages and currents, including

**Current gain:**  $\mathbf{H}_I(\omega) = \frac{\mathbf{I}_{\text{out}}(\omega)}{\mathbf{I}_{\text{in}}(\omega)}, \quad (9.2a)$

**Transfer impedance:**  $\mathbf{H}_Z(\omega) = \frac{\mathbf{V}_{\text{out}}(\omega)}{\mathbf{I}_{\text{in}}(\omega)}, \quad (9.2b)$

and

**Transfer admittance:**  $\mathbf{H}_Y(\omega) = \frac{\mathbf{I}_{\text{out}}(\omega)}{\mathbf{V}_{\text{in}}(\omega)}. \quad (9.2c)$