

Concept Question 9-13: When is a series RLC circuit a first-order circuit, and when is it a second-order circuit?

Overall, the series RLC circuit behaves like a second-order circuit, but at frequencies much lower or much higher than the resonance frequency, the circuit behavior resembles those of first-order circuits.