

Concept Question 9-16: Why is it more practical to cascade multiple stages of active filters than to cascade multiple stages of passive filters?

By using buffers (voltage followers in Chapter 4) between successive stages of active filters, the cascading approach allows the designer to work with each stage separately and then combine all of the stages together to achieve the desired specifications.