

**Concept Question 9-17:** What determines the gain factors of the highpass and lowpass op-amp filters?

In both cases, the gain factor is determined by the ratio of the feedback resistor to that of the input resistor.