

**Concept Question 9-3:** When is a circuit in a resonance condition?

► Resonance is a condition that occurs when the input impedance or input admittance of a circuit *containing reactive elements* is purely real, and the angular frequency at which it occurs is called the *resonant frequency*  $\omega_0$ . ◀