

Concept Question 9-5: How is the scaling concept used in the design of resonant circuits and filters?

When designing a frequency filter, it often is convenient to start by designing a **prototype model** in which the elements have values on the order of ohms, henrys, and farads and then to scale the prototype circuit into a **practical circuit** that not only contains elements with realistic values but also provides the specified frequency response.