

Concept Question 9-6: What remains unchanged in (a) magnitude scaling alone and (b) frequency scaling alone?

- (a) In magnitude scaling alone, the frequency response remains unchanged.
- (b) In frequency scaling alone, the impedances of the circuit elements remain unchanged.